



# ARM Memory Interface

---

Arm Bus Signal, Single Memory Interface, Control signal and Different accessing ways





# ARM Bus Signals


---

Memory bus interface signals include the following:

- ❖ A 32 bit address bus
- ❖ A 32 bit bidirectional bus
- ❖ Signals specifying what kind of memory requirement (*mreq*, *seq*)
- ❖ Signals specifying direction and size of memory
- ❖ Bus Timing and control signals (*abe*, *ale*, *ape*, *dbe*, *lock*, *bl[3:0]*).



# A basic ARM Memory System(1/2)

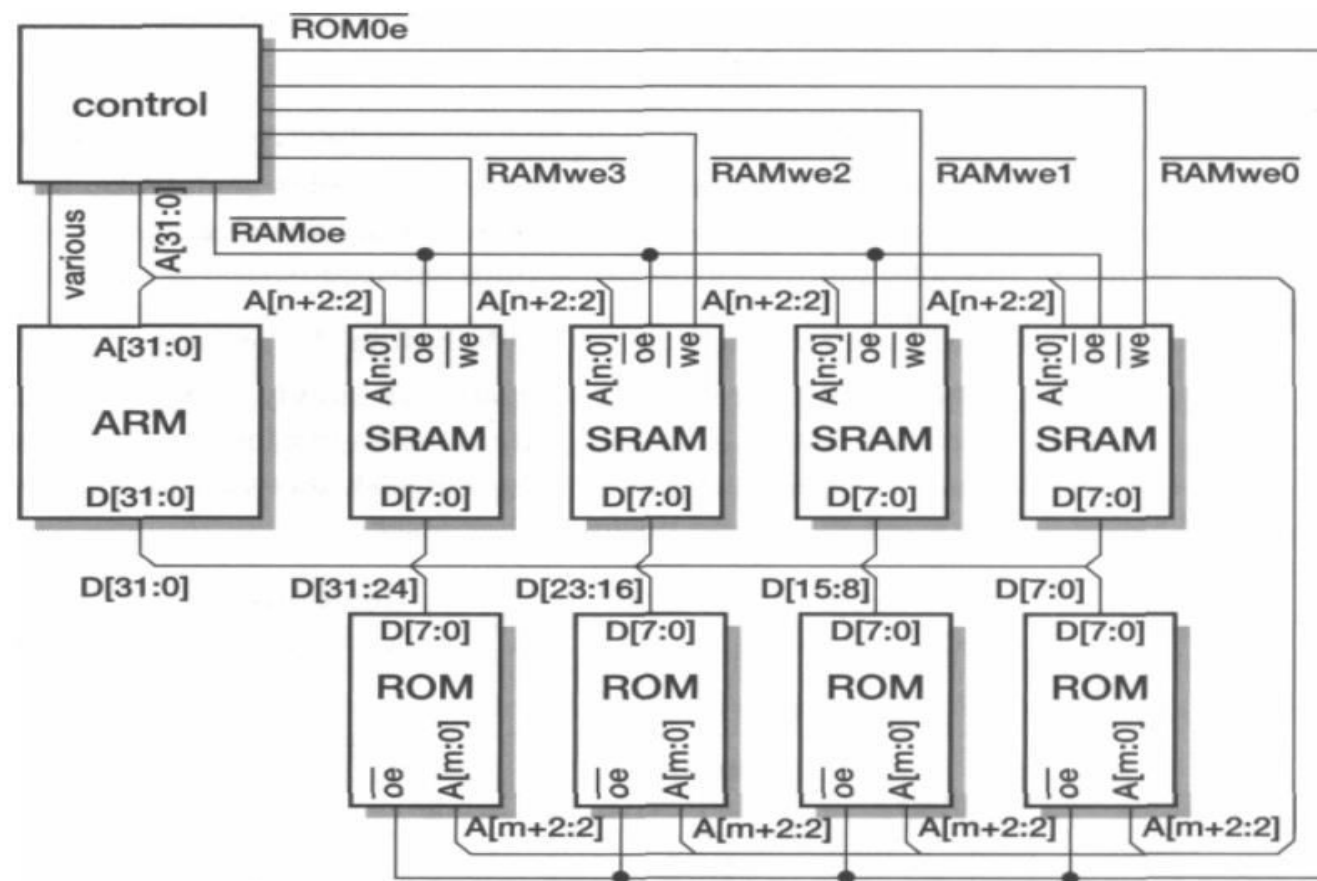



# A basic ARM Memory System(2/2)

---

- ❖ This figure illustrates the connection of 8-bit memory parts, which are a standard configuration for SRAMs and ROMs.
- ❖ The output enable signals (*RAMoe* and *ROMoe*) and the write enables (*RAMwe*) is seen in figure
- ❖ ROM can have a word access unlike RAM where separate enable for every 8 bit needed
- ❖ For ROM word access, [31:2] bits required, [1:0] can be used as control signals and for half word access [0] bit can be used for control signal.





# Control Logic

---

It performs mainly three functions:

- ❖ It decides when to activate the RAM and when to activate the ROM.
- ❖ It controls the byte write enables during a write operation
- ❖ It ensures that the data is ready before the processor continues.







# Stretching Access cycles

---

- ❖ The ARM7TDMI processor does not contain any dynamic logic that relies on regular clocking to maintain the internal state. Therefore, there is no limit upon the maximum period for which **MCLK** can be stretched, or **WAIT state** held LOW. There are two methods available to stretch access times as described in:
  - *Modulating MCLK*
  - *Use of WAIT state to control bus cycles.*






## ➤ Modulating MCLK

---

- ❖ All memory timing is defined by **MCLK**, and long access times can be accommodated by stretching this clock. It is usual to stretch the LOW period of **MCLK**, because this enables the memory manager to abort the operation if the access is eventually unsuccessful.
- ❖ **MCLK** can be stretched before being applied to the processor, or the **WAIT state** input can be used together with a free-running **MCLK**. Taking **WAIT state** LOW has the same effect as stretching the LOW period of **MCLK**.

## ➤ Wait States

 


ROM Wait control state transition diagram





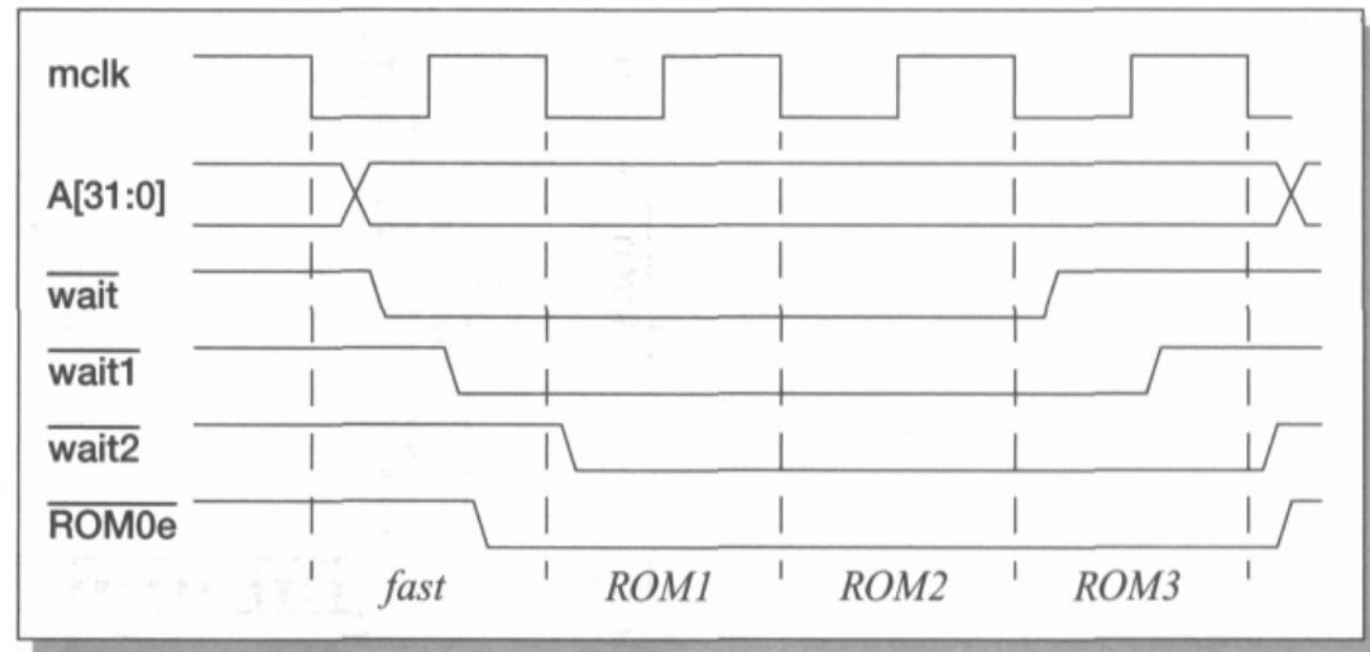
## The timing diagram for the ROM wait state logic


 
# Memory Access required or not?

- ❖ State transition diagram with a wait state for address decoding:






# Dynamic RAM (DRAM)

---

- ❖ Cheapest memory technology
- ❖ Stores information as electrical charge on capacitor
- ❖ Memory control logic refreshes the DRAM, so that information can be stored safely somewhere else.



# DRAM Memory organization(1/2)

 




# DRAM Memory organization(2/2)

---

- ❖ The row address is presented and latched using the active-low row **address strobe** signal (*ras*)
- ❖ The column address is presented and latched using the active-low **column address strobe** (*cas*)
- ❖ Very advantageous to use *cas-only* accesses whenever possible




# ARM Address Incrementor

 




# DRAM Timing Illustration

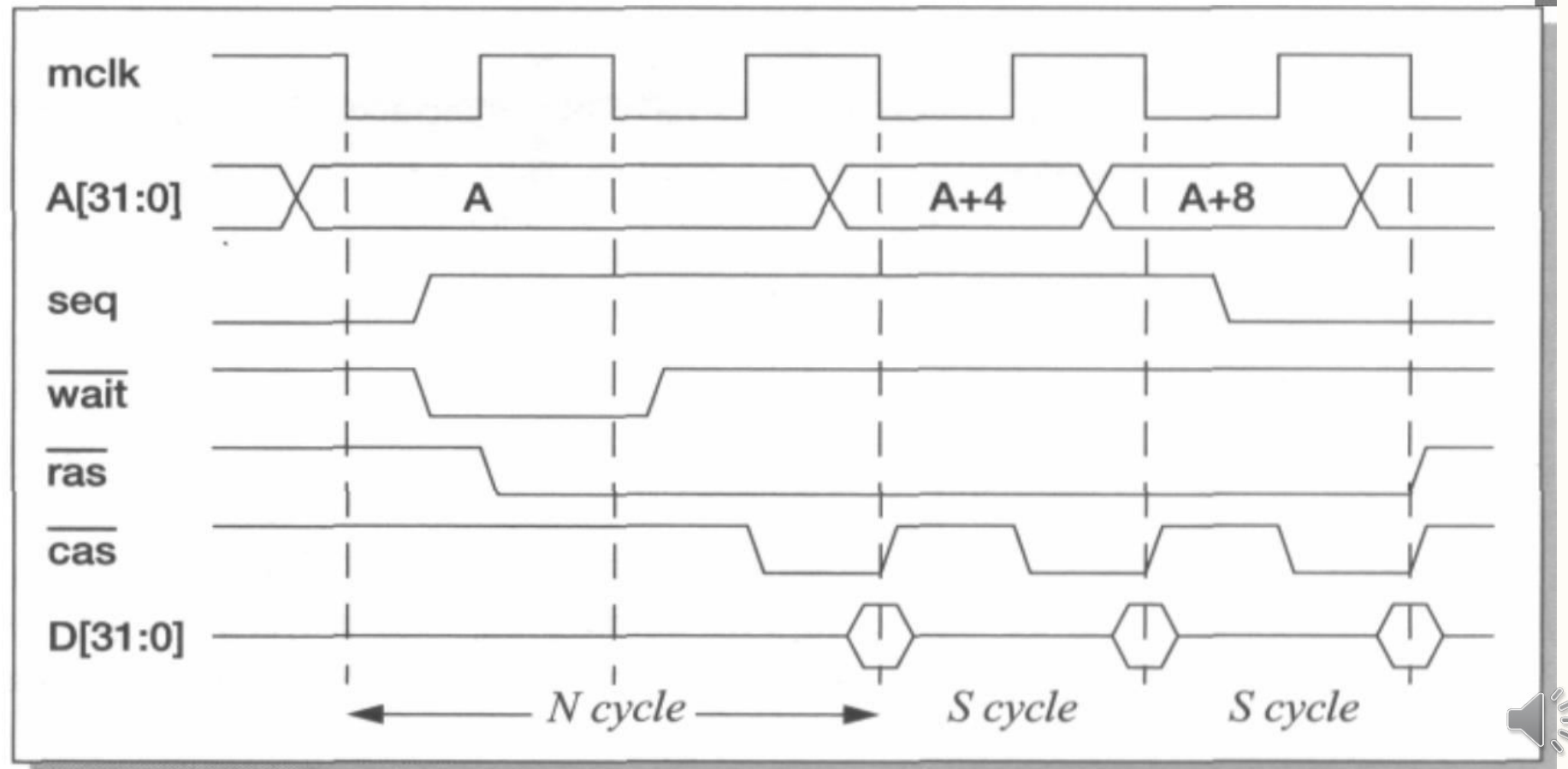

# DRAM timing after an internal cycle

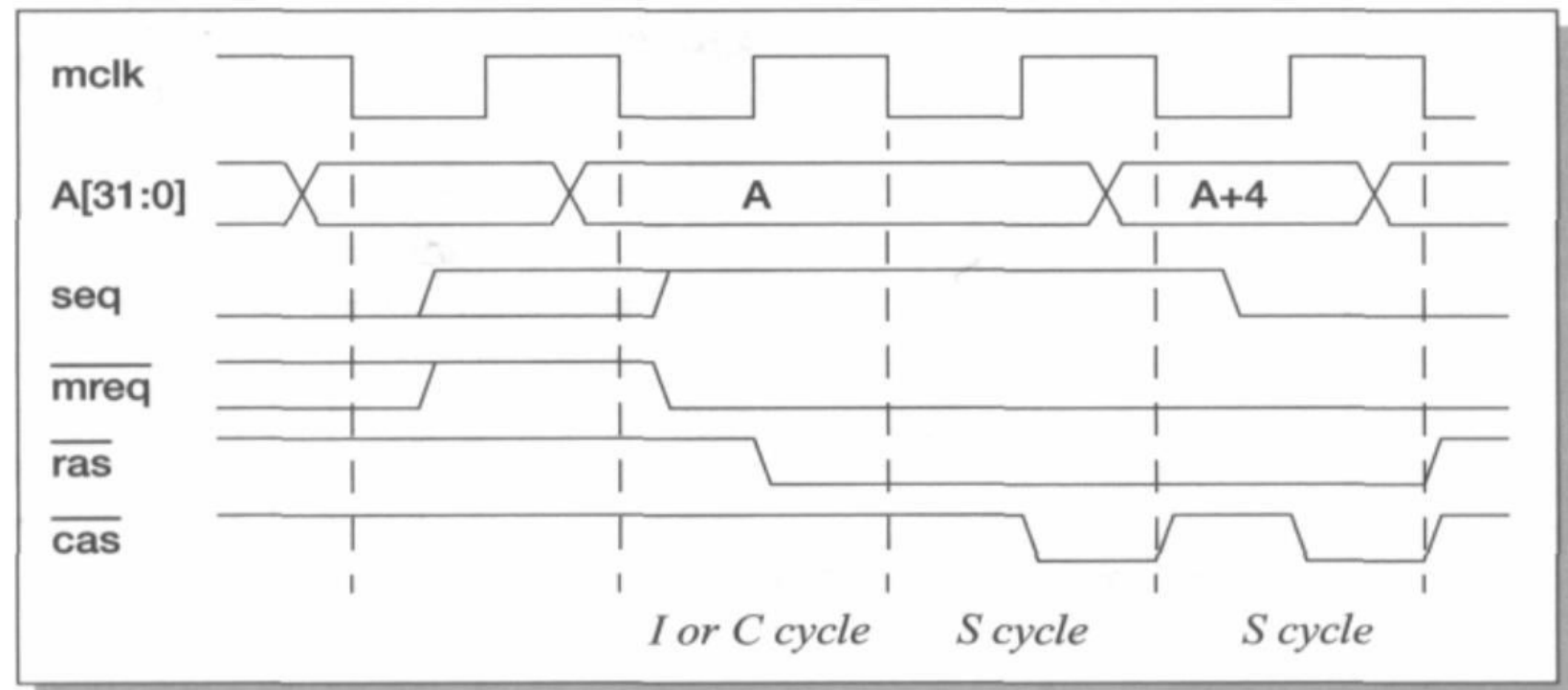

A decorative illustration of a pine branch with needles, rendered in a light green color, positioned on the left side of the slide.

# Thank You...!

---

